

ECE255 – Introduction to Digital Logic Design
Homework Assignment 5
Due November 13

Name: _____

1. Show how to use a **T FF** to *implement* a **D FF**.

- (a) First fill in the truth table below for next state Q^{t+1} for the D FF, then fill in the table for input T^t such that the T FF yields the correct next state (Q^{t+1}) for each row in the table.

D^t	Q^t	Q^{t+1}	T^t
0	0		
0	1		
1	0		
1	1		

- (b) T^t in the table you just completed is a function of D^t (the input) and Q^t (present state). This is a small state machine. Write the MSOP form for T^t . You may minimize to MSOP format any way you see fit.

MSOP $T(D^t, Q^t) =$

- (c) Sketch a schematic for this state machine showing the combinational logic for T^t and also the T FF with Q output. Draw by hand or use Logisim to sketch your circuit schematic.

2. Show how to use a **JK FF** to *implement* a **T FF**.

- (a) First fill in the truth table below for next state Q^{t+1} for the JK FF, then fill in the table for inputs J^t and K^t such that the JK FF yields the correct next state (Q^{t+1}) for each row in the table.

T^t	Q^t	Q^{t+1}	J^t	K^t
0	0			
0	1			
1	0			
1	1			

- (b) J' and K' in the table you just completed are functions of T' (the input) and Q' (present state). This is a small state machine. Write the MSOP forms for J' and K' . You may minimize to MSOP format any way you see fit.

MSOP $J(T', Q') =$

MSOP $K(T', Q') =$

- (c) Sketch a schematic for this state machine showing the combinational logic for inputs J' , K' and also the JK FF with Q output. Draw by hand or use Logisim to sketch your circuit schematic.

3. You are provided the following state table (assume 1-bit output z ; state assignments in parentheses):

	x	
	0	1
$A (00)$	$D/1$	$B/0$
$B (01)$	$D/1$	$C/0$
$C (10)$	$D/1$	$A/0$
$D (11)$	$B/1$	$C/0$

- (a) Construct a state diagram for the state table shown.

- (b) What is the Boolean logic equation for the output variable z ?