## **Example CSOP**

• Fill in the Truth Table and write Boolean expression for function  $f(X, Y, Z) = \sum_{1}^{\infty} (m_1, m_2, m_3, m_4, m_5, m_6, m_7)$ 

Mox+Y+Z

• Then write as CPOS form

XYZ	<u></u>
0 0 0	0←
001	1
010	1
0 1 1	l
100	1
101	1
011	\
( ) )	1



## **Example CPOS**

- Fill in the Truth Table and write Boolean expression for function  $g(X, Y, Z) = \prod_{1}(M_0, M_1, M_2, M_3, M_4, M_5, M_6)$
- Then write as CSOP form

$$g = \sum (m_7)$$
  
 $= \times YZ$   
 $t$   
 $CSOP$   
 $MSOP$ 

XYZ	g
200	0
001	0
010	J
DII	Ō
) 00	Ō
101	O
10	0
- 1 1 1	\ <del>\</del>



## **Example: CSOP and CPOS from Truth Table**


- Consider the Truth Table below for the function *f*
- Write out all minterms as "products" and all Maxterms as "sums"
- Write the CSOP using m-notation
- Write the CPOS using M-notation

·	,				Used	Used	$f=\sum (m_1, m_3, m_1)$
1) A	а	b	C	f	minterms	Maxterms	J-2 (M1, M3, M1
Mo-	0	0	0	0		atbtc	m - m
$m_{i}$	0	0	1	0 1	ā.b.c	0(151)	$M_{\xi}, M_{\gamma})$
MZ	0	1	0	<u>Q</u>		a+5+c	
M>	0	1	1	1	ābc		
M4	1	0	0	1	abc		= TT (Mo, Mz, M
M5		0	1	0	ω b C	a+6+2	- 11 (10 10) 10(z/V)
mb	1	1	0	1_	abī	001210	
M7		1	1	1	abc		



## **Basic Logic Gates**



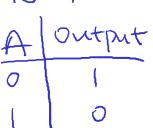



AND

A	В	Output
0	0	0
0	1	0
1	0	0
1	1	1




OR

A	В	Output
0	0	0
0	1	1
1	0	1
1	1	1



XOR

A	В	Output
0	0	0
0	1	1
1	0	1
1	1	0

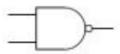

NAND

Α	В	Output
0	0	1
0	1	1
1	0	1
1	1	0



NOR

A	В	Output
0	0	1
0	1	0
1	0	0
1	1	0



**XNOR** 

A	В	Output
0	0	1
0	1	0
1	0	0
1	1	1



