

ECE255 – Introduction to Digital Logic Design
Homework Assignment 2
Due September 18

Min terms = 1
 Max terms = 0

Name: Isaac Abella

NOTE: Some questions require drawing schematics. You can use Logisim Evolution for drawing a schematic and then take a screenshot. Please see the Logisim Tutorial on Canvas as needed.

Let $ABCD_2$ be a 4-bit non-negative integer with corresponding decimal values:

$0000_2 = 0_{10}$
 $0001_2 = 1_{10}$
 $0010_2 = 2_{10}$
 $0011_2 = 3_{10}$
 \dots
 $1111_2 = 15_{10}$

The digits A, B, C , and D in this 4-bit integer are also to be considered variables. Consider two functions of these 4 variables $f(A, B, C, D)$ and $g(A, B, C, D)$.

1. The function $f(A, B, C, D)$ is defined as:

$$f = \begin{cases} 1 & \text{if the hex value of } ABCD_2 \text{ is less than } A_{16} \\ 0 & \text{otherwise} \end{cases}$$

We have 4^n calculations
 outputs true = 1
 false = 0

Describe f in the following forms listed below:

- (a) Truth Table → when 0
 (b) CSOP in the concise $\sum m_i$ notation
 (c) CPOS in the concise $\prod M_i$ notation ← when 1

CSOP in $\sum m_i$ notation

① Truth Table 16 bit

input				output	
A	B	C	D	f	g
m_0	0	0	0	1	0
m_1	0	0	1	1	0
m_2	0	0	1	1	0
m_3	0	0	1	1	0
m_4	0	1	0	1	0
m_5	0	1	0	1	0
m_6	0	1	1	1	0
m_7	0	1	1	1	0
m_8	1	0	0	1	0
m_9	1	0	0	1	0
m_{10}	1	0	1	0	1
m_{11}	1	0	1	0	1
m_{12}	1	1	0	0	1
m_{13}	1	1	0	0	1
m_{14}	1	1	1	0	1
m_{15}	1	1	1	0	1

1 if hex of $ABCD_2$ is less
 than A_{16} , if $>$, then it's 0

A_{16} is 1010_2 so everything
 after is 0 but all before are 1.

② CPOS $\prod M_i$ notation

$$= \prod (m_0, m_1, m_2, m_3, m_4, m_5, m_6, m_7, m_8, m_9)$$

③ CSOP $\sum m_i$ notation

$$= \sum (m_{10}, m_{11}, m_{12}, m_{13}, m_{14}, m_{15})$$

2. The function $g(A, B, C, D)$ is defined as:

$$g = \begin{cases} 0 & \text{if } f=1 \\ 1 & \text{if } f=0 \end{cases}$$

Describe g in the following forms listed below:

- (a) CSOP in the concise $\sum m_i$ notation
(b) CPOS in the concise $\prod M_i$ notation

(A) CSOP in $\sum m_i$ notation

$$\prod (m_{10} m_{11} m_{12} m_{13} m_{14} m_{15})$$

(B) CPOS $\sum (m_0 m_1 m_2 m_3 m_4 m_5 m_6 m_7 m_8 m_9)$

input				output	
A	B	C	D	f	g
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	0	1

3. Express the function $f(A, B, C, D)$ in the following forms:

- (a) A Boolean Algebra expression of the CSOP function $f(A, B, C, D)$
(b) A minimized Boolean expression for $f(A, B, C, D)$

Use the properties and axioms of Boolean Algebra to minimize $f(A, B, C, D)$

$$X + X' = 1$$

$$X \cdot X' = 0$$

input				output		terms
A	B	C	D	f	g	min term
0	0	0	0	1	0	$A \cdot B \cdot C \cdot D$ m_0
0	0	0	1	1	0	$A \cdot B \cdot C \cdot \bar{D}$ m_1
0	0	1	0	1	0	$A \cdot B \cdot \bar{C} \cdot D$ m_2
0	0	1	1	1	0	$A \cdot B \cdot \bar{C} \cdot \bar{D}$ m_3
0	1	0	0	1	0	$A \cdot \bar{B} \cdot C \cdot D$ m_4
0	1	0	1	1	0	$A \cdot \bar{B} \cdot C \cdot \bar{D}$ m_5
0	1	1	0	1	0	$A \cdot \bar{B} \cdot \bar{C} \cdot D$ m_6
0	1	1	1	1	0	$A \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}$ m_7
1	0	0	0	1	0	$\bar{A} \cdot B \cdot C \cdot D$ m_8
1	0	0	1	1	0	$\bar{A} \cdot B \cdot C \cdot \bar{D}$ m_9
1	0	1	0	0	1	$\bar{A} \cdot B \cdot \bar{C} \cdot D$ m_{10}
1	0	1	1	0	1	$\bar{A} \cdot B \cdot \bar{C} \cdot \bar{D}$ m_{11}
1	1	0	0	0	1	$\bar{A} \cdot \bar{B} \cdot C \cdot D$ m_{12}
1	1	0	1	0	1	$\bar{A} \cdot \bar{B} \cdot C \cdot \bar{D}$ m_{13}
1	1	1	0	0	1	$\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D$ m_{14}
1	1	1	1	0	1	$\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}$ m_{15}

CSOP \rightarrow

$A \cdot B \cdot C \cdot D$ m_0
 $A \cdot B \cdot C \cdot \bar{D}$ m_1
 $A \cdot B \cdot \bar{C} \cdot D$ m_2
 $A \cdot B \cdot \bar{C} \cdot \bar{D}$ m_3
 $A \cdot \bar{B} \cdot C \cdot D$ m_4
 $A \cdot \bar{B} \cdot C \cdot \bar{D}$ m_5
 $A \cdot \bar{B} \cdot \bar{C} \cdot D$ m_6
 $A \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}$ m_7
 $\bar{A} \cdot B \cdot C \cdot D$ m_8
 $\bar{A} \cdot B \cdot C \cdot \bar{D}$ m_9
 $\bar{A} \cdot B \cdot \bar{C} \cdot D$ m_{10}
 $\bar{A} \cdot B \cdot \bar{C} \cdot \bar{D}$ m_{11}
 $\bar{A} \cdot \bar{B} \cdot C \cdot D$ m_{12}
 $\bar{A} \cdot \bar{B} \cdot C \cdot \bar{D}$ m_{13}
 $\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D$ m_{14}
 $\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}$ m_{15}

Can't be a 3 term product.

$$f = (\bar{A} \bar{B} \bar{C} \bar{D}) + (\bar{A} \bar{B} \bar{C} D) + (\bar{A} \bar{B} C \bar{D}) + (\bar{A} \bar{B} C D) + (\bar{A} B \bar{C} \bar{D}) + (\bar{A} B \bar{C} D) + (\bar{A} B C \bar{D}) + (\bar{A} B C D) + (A \bar{B} \bar{C} \bar{D}) + (A \bar{B} \bar{C} D) + (A \bar{B} C \bar{D}) + (A \bar{B} C D) + (A B \bar{C} \bar{D}) + (A B \bar{C} D) + (A B C \bar{D}) + (A B C D)$$

$$= \bar{A} \bar{B} \bar{C} (\bar{D} + D) + \bar{A} \bar{B} C (\bar{D} + D)$$

$$= \bar{A} \bar{B} \bar{C} (\bar{D} + D) + \bar{A} \bar{B} C (\bar{D} + D)$$

$$+ \bar{A} \bar{B} \bar{C} (\bar{D} + D)$$

$$= \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} B \bar{C} + \bar{A} B C + A \bar{B} \bar{C} + A \bar{B} C + A B \bar{C} + A B C$$

$$= \bar{A} \bar{B} (\bar{C} + C) + \bar{A} B (\bar{C} + C) + A \bar{B} \bar{C} + A B \bar{C}$$

$$= \bar{A} \bar{B} + \bar{A} B + A \bar{B} \bar{C} + A B \bar{C}$$

$$= \bar{A} (\bar{B} + B) + A \bar{B} \bar{C} + A B \bar{C}$$

$$= \bar{A} + A \bar{B} \bar{C} + A B \bar{C}$$

5 gates

not, 1 or, 1 and.

$$\boxed{= \bar{A} + \bar{B} \bar{C}}$$

4. Express $f(A, B, C, D)$ as a digital logic schematic, clearly showing AND, NOT, and OR gates used and how they are connected. Draw by hand or use Logisim to place and connect gates.

$$f(A, B, C, D) = \bar{A} + \bar{B}\bar{C} \quad \text{3 not inputs feed}$$

$$(\text{NOT } A) \text{ OR } (\text{NOT } B \text{ AND NOT } C)$$

invert A, B, C and put BC into a NAND Gate before doing A OR B

$$\text{NOT } A \Rightarrow A(1)$$

$$B \text{ NAND } C = 0$$

