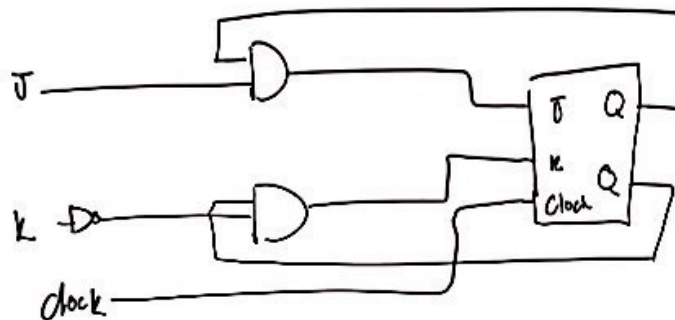


- (b) J' and K' in the table you just completed are functions of T' (the input) and Q' (present state). This is a small state machine. Write the MSOP forms for J' and K' . You may minimize to MSOP format any way you see fit.

$$\text{MSOP } J(T', Q') = \overline{T'} Q' (m_2)$$

$$\text{MSOP } K(T', Q') = \overline{T'} Q' (m_1)$$


- (c) Sketch a schematic for this state machine showing the combinational logic for inputs J' , K' and also the JK FF with Q output. Draw by hand or use Logisim to sketch your circuit schematic.



3. You are provided the following state table (assume 1-bit output z ; state assignments in parentheses):

	x	
	0	1
$A(00)$	$D/1$	$B/0$
$B(01)$	$D/1$	$C/0$
$C(10)$	$D/1$	$A/0$
$D(11)$	$B/1$	$C/0$

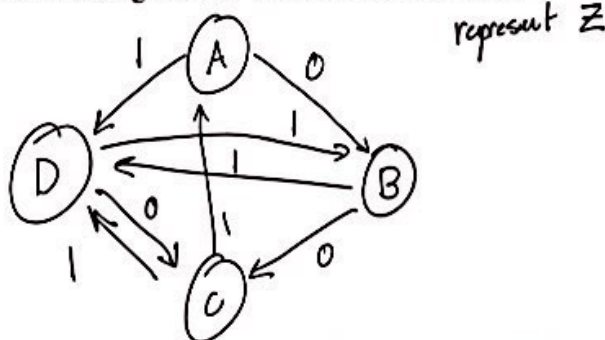- (a) Construct a state diagram for the state table shown.



- (b) What is the Boolean logic equation for the output variable z ?

$$z = \overline{x}$$