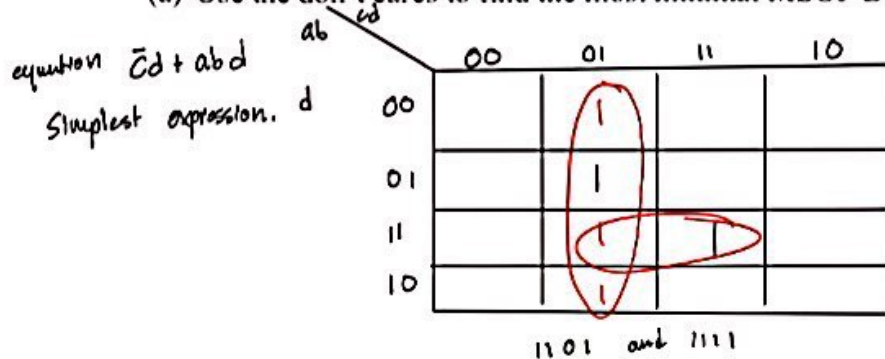


ECE255 – Introduction to Digital Logic Design
Homework Assignment 3
Due September 22

Name: Isaac Abula 9/25/23

1. You are given the function $f(a, b, c, d) = \sum(m_5, m_{15}) + \sum d(m_1, m_9, m_{13})$ with 2 minterms and 3 don't cares.

(a) Use the don't cares to find the most minimal MSOP Boolean expression for f using a K-map.




We can turn the don't cares to ones and get a group of 4 and 1 2 group for the MSOP.

- (b) Using the MSOP form from (a), use the Boolean Algebra rules to further minimize f in terms of fewer gates required and fewer inputs per logic gate. **Show your work.**


my boolean algebra solution is the simplest it can go.

$\bar{c}d + ABD$

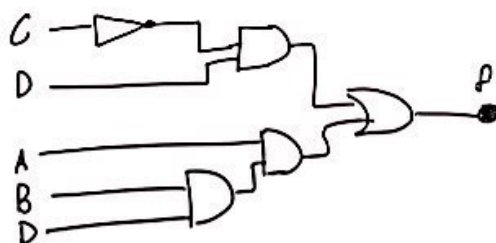

- 1 inverter
- 3 AND gates
- 1 OR gate
- 1 Led output.

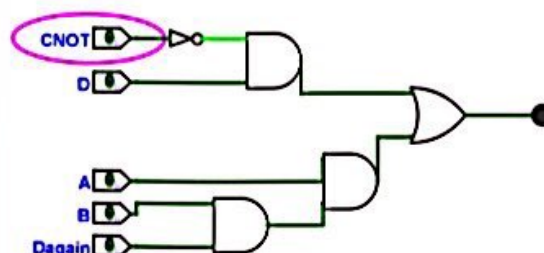
- (c) Sketch (or use Logisim) a schematic of the digital circuit that implements your Boolean function from (b).




2. Consider the application of De Morgan's Laws to **implement a digital circuit consisting of only NAND gates**. You may assume complemented inputs to the function are already available.

You are given the function $f(a, b, c) = \sum(m_3, m_4, m_6, m_7)$.

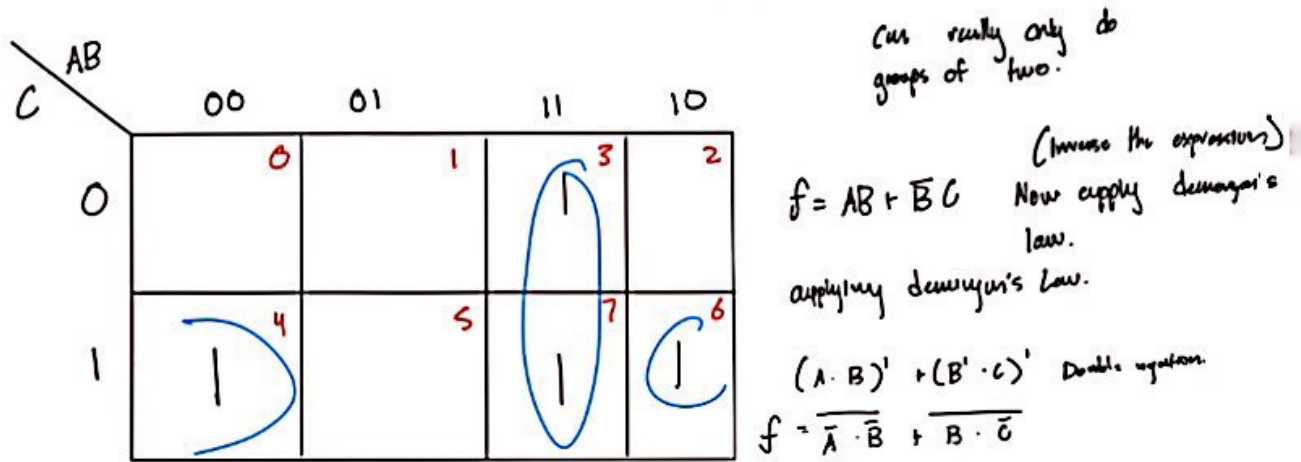- (a) Determine a Boolean expression for f in terms of NAND gates only. Hint: Start with a K-map to find the MSOP and then convert to a NAND based solution by applying De Morgan's Theorem.



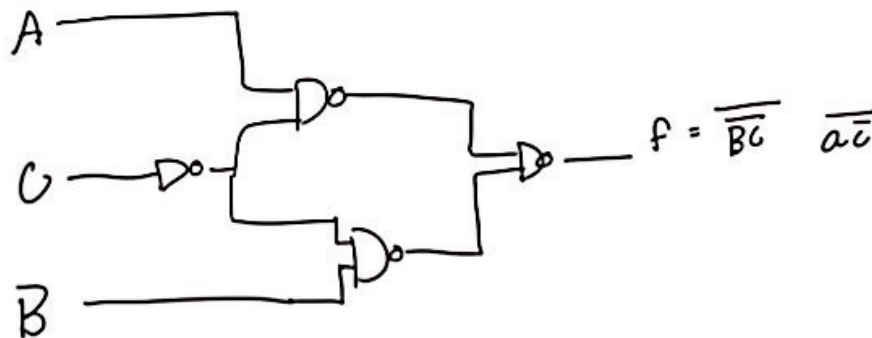- (b) Sketch (or use Logisim) a schematic of the digital circuit that implements your NAND-based Boolean function from (a).



3. You are given the function $f(a, b, c, d) = \sum(m_1, m_4, m_7, m_{14}, m_{15}) + \sum d(m_0, m_5, m_9)$.

(a) Use a K-map to determine the MSOP form for f .

0111
1111

| | | | | | |
|----|--|---------|---------|---------|---------|
| | | 00 | 10 | 11 | 10 |
| 00 | | 0 X | 1 1 | 3 1 | 2 1 |
| 01 | | 4 1 | 5 X | 7 1 | 6 1 |
| 11 | | 12 1 | 13 1 | 15 1 | 14 1 |
| 10 | | 8 1 | 9 X | 11 1 | 10 1 |

We can form m_0 and m_5 to simplify a group of 4; but m_9 is useless.

group m_5, m_7 and overlap m_5, m_{14} as that's the simplest.

1111
1110

$$f = \bar{a}\bar{c} + ABC + \bar{A}BD \quad \text{now simplify.}$$

(b) Sketch (or use Logisim) a schematic of the digital circuit that implements your NAND-based Boolean function from (a).

NAND Based

$$f = \overline{(\overline{ABC} + \overline{BCD} + \overline{\bar{A}\bar{C}})}$$

$$= \overline{\overline{ABC}} + \overline{\overline{BCD}} + \overline{\overline{\bar{A}\bar{C}}}$$

